

CPLD 設計作業

範圍： State machine

銘傳大學電腦與通訊工程系

班 級	電通四甲
姓 名	余采潔
學 號	05051115
作業成果	應繳作業共 <u>2</u> 題，每題 50 分 我共完成 <u>2</u> 題，應得 <u>100</u> 分
授課教師	陳慶逸

■ 請確實填寫自己寫完成題數，填寫不實者(如上傳與作業明顯無關的答案，或是計算題數有誤者)，本次作業先扣 50 分。


第一題

實現一個 1Hz 頻率計數的 3 bits 計數器：

1. 可控制上、下數計數的 3 位元計數器。
2. 計數頻率為 1Hz。
3. 在 DE0 實驗板上實現本電路功能要求。

本題應包含 DE0 實驗板驗證,執行結果請以影片播放方式 Demo(可上傳至 youtube 並設為公開,然後並在實驗報告上提供連結至 youtube 影片的網址)。

最上層設計的電路圖擷圖：

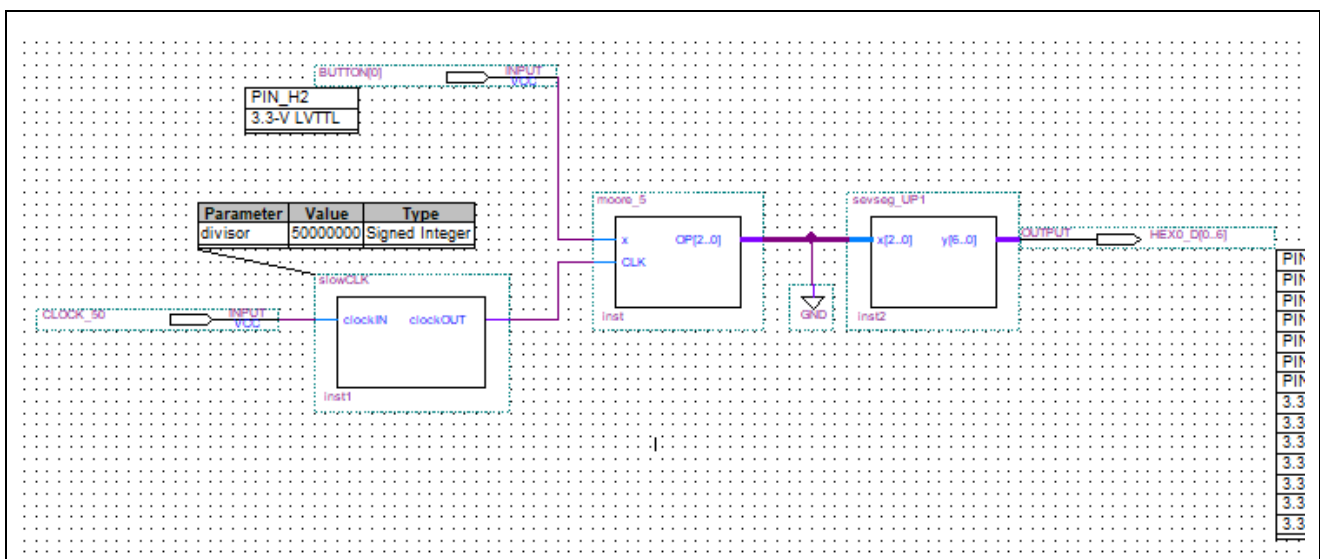

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_unsigned.all;

ENTITY moore_5 IS
PORT(  x,CLK :IN STD_LOGIC;
      OP      :OUT std_logic_vector(2 downto 0));
END moore_5;

ARCHITECTURE a OF moore_5 IS
BEGIN
PROCESS(clk)
```

```
variable present_state: std_logic_vector (2 downto 0);
BEGIN
  IF clk'event and clk='1' then
    CASE present_state IS
      WHEN "000" =>
        if x='1' then  present_state:="001";
        else present_state:="111";
        end if;
      WHEN "001" =>
        if x='1' then  present_state:="010";
        else present_state:="000";
        end if;
      WHEN "010" =>
        if x='1' then  present_state:="011";
        else present_state:="001";
        end if;
      WHEN "011" =>
        if x='1' then  present_state:="100";
        else present_state:="010";
        end if;
      WHEN "100" =>
        if x='1' then  present_state:="101";
        else present_state:="011";
        end if;
      WHEN "101" =>
        if x='1' then  present_state:="110";
        else present_state:="100";
        end if;
      WHEN "110" =>
        if x='1' then  present_state:="111";
        else present_state:="101";
        end if;
      WHEN "111" =>
        if x='1' then  present_state:="000";
        else present_state:="110";
        end if;
      WHEN others=>
        if x='1' then  present_state:="000";
        else present_state:="000";
        end if;
```


```
        END CASE;  
    end if;  
    op<= present_state;  
END PROCESS;  
END a;
```

影片連結網址:

<https://youtu.be/Pr7DSpirNC4>

第二題

請實現下面的狀態機電路。

 

程式碼:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_unsigned.all;

ENTITY zxc IS
PORT(CLK :IN STD_LOGIC;
      X   :IN STD_LOGIC;
      op  :OUT STD_LOGIC);
END zxc;

ARCHITECTURE a OF zxc IS
TYPE State IS (s0,s1,s2,s3,s4);
SIGNAL present_state : State;
SIGNAL next_state: State;
BEGIN
    state_comp: PROCESS(present_state)
    BEGIN
        CASE present_state IS
            WHEN s0 =>
                IF X = '0' THEN
                    next_state <= s0;
                ELSE
                    next_state <= s1;
                END IF;
            WHEN s1 =>
                IF X = '0' THEN
                    next_state <= s2;
                ELSE
                    next_state <= s3;
                END IF;
            WHEN s2 =>
                IF X = '0' THEN
                    next_state <= s4;
                ELSE
                    next_state <= s0;
                END IF;
            WHEN s3 =>
                IF X = '0' THEN
                    next_state <= s1;
                ELSE
                    next_state <= s2;
                END IF;
            WHEN s4 =>
                IF X = '0' THEN
                    next_state <= s3;
                ELSE
                    next_state <= s4;
                END IF;
        END CASE;
    END PROCESS;
    present_state <= next_state;
    op <= '1';
END a;
```

```
IF X = '0' THEN
    op <= '0';
ELSE
    op <= '0';
END IF;
```

```
WHEN s1 =>
    IF X = '0' THEN
        next_state <= s2;
    ELSE
        next_state <= s3;
    END IF;
    IF X = '0' THEN
        op <= '0';
    ELSE
        op <= '0';
    END IF;
```

```
WHEN s2 =>
    IF X = '0' THEN
        next_state <= s4;
    ELSE
        next_state <= s0;
    END IF;
    IF X = '0' THEN
        op <= '0';
    ELSE
        op <= '1';
    END IF;
```

```
WHEN s3 =>
    IF X = '0' THEN
        next_state <= s1;
    ELSE
        next_state <= s2;
    END IF;
    IF X = '0' THEN
        op <= '1';
    ELSE
        op <= '1';
    END IF;
```

```

WHEN s4 =>
    IF X = '0' THEN
        next_state <= s3;
    ELSE
        next_state <= s4;
    END IF;
    IF X = '0' THEN
        op <= '1';
    ELSE
        op <= '1';
    END IF;

END CASE;
END PROCESS state_comp;

```

```

state_clocking: PROCESS (CLK)
BEGIN
    IF CLK'EVENT AND CLK = '1' THEN
        present_state <= next_state;
    END IF;
END PROCESS state_clocking;

```

END a;

模擬結果:

