

CPLD 設計作業

範圍： Data flow description

銘傳大學電腦與通訊工程系

班 級	電通四甲
姓 名	余采潔
學 號	05051115
作業成果	應繳作業共 <u>10</u> 題，每題 10 分 我共完成 <u>10</u> 題，應得 <u>100</u> 分
授課教師	陳慶逸

■ 請確實填寫自己寫完成題數，填寫不實者(如上傳與作業明顯無關的答案，或是計算題數有誤者)，本次作業先扣 50 分。

第一題

問題描述: 利用 VHDL 以及時序模擬的結果證明 $x(x'+y) = xy$

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
  port ( x,y: in STD_LOGIC;
         F1,F2 : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

  F1<=x and ((not x) or y);
  F2<=x and y;

end arch;
```

模擬結果擷圖:

 

第二題

問題描述: 利用 VHDL 以及時序模擬的結果證明 $x+x'y = x+y$

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
port ( x,y: in STD_LOGIC;
      F1,F2 : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

    F1<=x or (not(x)and y);
    F2<=x or y;

end arch;
```

模擬結果擷圖:

 

第三題

問題描述: 利用 VHDL 以及時序模擬的結果證明 $(x+y)(x+y') = x$

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
port ( x,y: in STD_LOGIC;
      F1,F2 : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

    F1<=(x or y) and (x or not(y)) ;
    F2<=x ;

end arch;
```

模擬結果擷圖:

 

第四題

問題描述: 利用 VHDL 以及時序模擬的結果證明 $xy + x'z + yz = xy + x'z$

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
port ( x,y,z: in STD_LOGIC;
      F1,F2 : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

    F1<=(x and y) or (not(x) and z) or (y and z) ;
    F2<=(x and y) or (not(x) and z);

end arch;
```

模擬結果擷圖:

 

第五題

問題描述: 利用 VHDL 以及時序模擬的結果證明 $(x+y)(x'+z)(y+z)=(x+y)(x'+z)$

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
port ( x,y,z: in STD_LOGIC;
      F1,F2 : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

    F1<=(x or y) and (not(x) or z) and (y or z) ;
    F2<=(x or y) and (not(x) or z);

end arch;
```

模擬結果擷圖:

 

第六題

問題描述: 利用 VHDL 以及時序模擬的結果證明下面的真值表中, $F = \Sigma(1,4,5,6,7)$

和 $F = \text{not}(\Sigma(0,2,3))$ 的輸出結果是相同的。

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
port ( x,y,z: in STD_LOGIC;
      F1,F2 : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

  F1<=(not(x) and not(y) and z )
    or (x and not(y) and not(z) )
    or (x and not(y) and z )
    or (x and y and not(z) )
    or (x and y and z);
  F2<=not((not(x) and not(y) and not(z) )
    or (not(x) and y and not(z) )
    or (not(x) and y and z));
```

```
end arch;
```

模擬結果擷圖：

 

第七題

問題描述:下面真值表中，請以 product of maxterms 來表示 f_1 的輸出，並以 sum of minterms 來表示 f_2 的輸出。最後，請利用 VHDL 來描述 f_1 和 f_2 ，並完成時序模擬。

Functions of Three Variables

x	y	z	Function f_1	Function f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity abc is
port ( x,y,z: in STD_LOGIC;
      F1,F2 : out STD_LOGIC);
end abc;


architecture arch of abc is
begin

  F1<=(x or y or z )
    and (x or not(y) or z )
    and (x or not(y) or not(z))
    and (not(x) or y or not(z))
    and (not(x) or not(y) or z);
  F2<=(not(x) and y and z )
```

```
or (x and not(y) and z )  
or (x and y and not(z) )  
or (x and y and z );
```


```
end arch;
```

模擬結果擷圖：

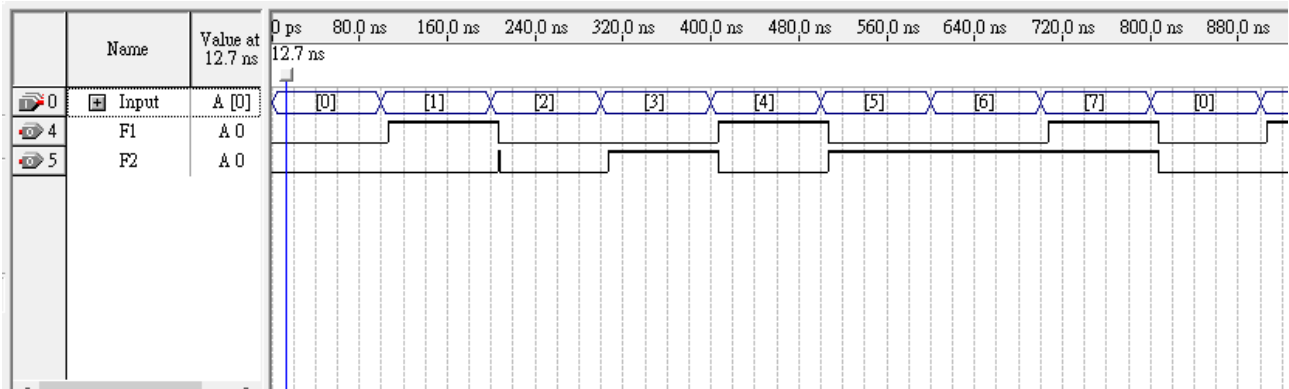

第八題

問題描述:請利用 VHDL 來描述下面電路，並完成時序模擬。

 

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
port ( x,y: in STD_LOGIC;
      F1,F2 : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

  F1<=(x and not(y))
    or (not(x) and y);
  F2<=(x nand (x nand y))
    nand((x nand y)nand y);


end arch;
```

模擬結果擷圖：

 

第九題

問題描述:請利用 VHDL 來描述下面電路，並完成時序模擬。

 

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;


entity abc is
port ( x,y,z: in STD_LOGIC;
      S,C : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

    S<=(x xor y) xor z;
    C<=((x xor y)and z)
      or(x and y);


end arch;
```

模擬結果擷圖:

 

第十題

問題描述:請利用 VHDL 來描述下面電路，並完成時序模擬。

 

程式碼:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity abc is
port ( x,y,z: in STD_LOGIC;
      F : out STD_LOGIC);
end abc;

architecture arch of abc is
begin

    F<=(x and not(z)) or (y and z);

end arch;
```

模擬結果擷圖:

