

CPLD 設計作業

範圍：Hierarchical Design

銘傳大學電腦與通訊工程系

班 級	電通四甲
姓 名	余采潔
學 號	
作業成果	應繳作業共 <u>3</u> 題，前 2 題每題 30 分，第 3 題 40 分 我共完成 <u>3</u> 題，應得 <u>100</u> 分
授課教師	陳慶逸


■ 請確實填寫自己寫完成題數，填寫不實者(如上傳與作業明顯無關的答案，或是計算題數有誤者)，本次作業先扣 50 分。

第一題

利用階層式設計實現一個半加法器(h_adder.vhd)。

(互斥或閘: xor_2.vhd, 及閘: and_2.vhd)。

作業應包含程式碼及模擬圖。

 

XOR

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity xor_2 is
```

```
port ( X,Y :in std_logic;
```

```
      S :out std_logic);
```

```
end xor_2;
```

```
ARCHITECTURE a OF xor_2 IS
```

```
begin
```

```
S<=X xor Y;
```

```
end a;
```

AND

```
library ieee;
use ieee.std_logic_1164.all;
entity and_2 is
port ( M,Z :in std_logic;
C :out std_logic);
end and_2;
ARCHITECTURE a OF and_2 IS
begin
C<=M and Z;
end a;
```

h_adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
ENTITY h_adder IS
PORT ( a,b : IN STD_LOGIC;
Sum,carry : out STD_LOGIC);
END h_adder;
ARCHITECTURE a OF h_adder IS
component xor_2
port ( X,Y :in std_logic;
S : out std_logic );
end component;
component and_2
port ( M,Z :in std_logic;
```

```
C :out std_logic );
```

```
end component;
```

```
begin
```

```
U1:xor_2 port map (a,b,Sum);
```


```
U2:and_2 port map (a,b,carry);
```

```
END a;
```

第二題

利用階層式設計實現一個 4-bit 加法器(add_4_bits.vhd)。

(1-bit 加法器: add_1_bit.vhd)。

 

add_1_bits

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
ENTITY add_1_bits IS
```

```
port
```

```
(a :in std_logic;
```

```
  b :in std_logic;
```

```
  ci:in std_logic;
```

```
  s :out std_logic;
```

```
  c :out std_logic);
```

```
end add_1_bits;
```

```
ARCHITECTURE a OF add_1_bits IS
```

```
begin
s<=a xor b xor ci;
c<=(a and b ) or (a and ci) or (b and ci);
end a;
```

add_4_bits

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
```

```
ENTITY add_4_bits IS
PORT ( x : in STD_LOGIC_vector(3 downto 0);
y : in STD_LOGIC_vector(3 downto 0);
cin : in STD_LOGIC;
sum: out std_logic_vector(3 downto 0);
cout: out std_logic);
END add_4_bits ;
```

```
ARCHITECTURE a OF add_4_bits IS
```

```
component add_1_bits
```

```
port
```

```
(
```

```
a :in std_logic;
```

```
b :in std_logic;
```

```
ci:in std_logic;
```

```
s :out std_logic;
```

```
c :out std_logic
```

);

end component;

signal s1,s2,s3,s4 : std_logic;

BEGIN

IC1:add_1_bits port map(a=>x(0),b=>y(0),c=>s1,s=>sum(0),ci=>cin);

IC2:add_1_bits port map(a=>x(1),b=>y(1),c=>s2,s=>sum(1),ci=>s1);

IC3:add_1_bits port map(a=>x(2),b=>y(2),c=>s3,s=>sum(2),ci=>s2);

IC4:add_1_bits port map(a=>x(3),b=>y(3),c=>cout,s=>sum(3),ci=>s3);

END a;

第三題

以 5 個四對一的多工器實現一個十六對一的多工器。

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY zxc IS
PORT (  D : IN STD_LOGIC_vector(0 to 15);
        S : IN  STD_LOGIC_vector(3 downto 0);
        Y : OUT STD_LOGIC);
END zxc ;

ARCHITECTURE a OF zxc IS
    component mux4_1
        port ( d0,d1,d2,d3 :in std_logic;
                S1,S2          :IN std_logic;
                Y              :out std_logic );
    end component;

    signal m :std_logic_vector(0 to 3);
BEGIN
    mux1:mux4_1 port map(D(0),D(1),D(2),D(3),S(1),S(0),m(0));
    mux2:mux4_1 port map(D(4),D(5),D(6),D(7),S(1),S(0),m(1));
    mux3:mux4_1 port map(D(8),D(9),D(10),D(11),S(1),S(0),m(2));
    mux4:mux4_1 port map(D(12),D(13),D(14),D(15),S(1),S(0),m(3));
    mux5:mux4_1 port map(m(0),m(1),m(2),m(3),S(3),S(2),Y);
```


END a;

mux4_1

library ieee;

use ieee.std_logic_1164.all;

entity mux4_1 is

port (d0,d1,d2,d3 :in std_logic;

 S1,S2 :IN std_logic;

 Y :out std_logic);

 end mux4_1;

ARCHITECTURE a OF mux4_1 IS

BEGIN

 process (S1,S2,d0,d1,d2,d3)

 begin

 if S1='0' and S2='0'then

 Y <= d0;

 elsif S1='0' and S2='1' then

 Y <= d1;

 elsif S1='1' and S2='0' then

 Y <= d2;

 elsif S1='1' and S2='1' then

```

        Y <= d3;

    end if;

    end process;

```

```

END a;

```

